

# Sound Level Meter

James Walker-Wilson

January 7, 2018

## Abstract

This report outlines the construction of a sound level meter and the testing of the meter, this meter is sensitive to sounds at  $1.5kHz$  and displays the sound level on a graph made of 10 LED's. This report outlines the theory behind the operation of the meter and the operation of the individual stages.

# 1 Introduction

This report outlines the design and construction of a sound level meter. The device measures the sound level of the environment. This is filtered through several filter stages and the sound level is displayed on an LED bar graph. The sound signal is filtered to select a band of frequencies and then low pass filtered to produce a DC voltage level proportional to the sound level.

## 1.1 Aims

- To understand the design of a common emitter amplifier for the first stage.
- To understand the design of an LC band pass filter.
- To understand the construction and operation of a signal rectifier.
- To understand the construction of a low pass filter.
- To understand how to program a PIC Micro controller.
- To understand the construction and testing of the circuit.

## 1.2 Objectives

- To determine the  $\beta$  of the transistor by experimentation
- To design a common emitter amplifier for the first stage of the circuit with appropriate gain
- To design an LC band pass filter and calculate the number of turns of wire to create the required inductance.
- To construct a rectifier to rectify the signal
- To construct a low pass filter to convert the signal to a dc voltage level.
- To create a program to change the number of LED's that are on depending on the sound level and program the Micro controller with the code.
- To test the completed stages and whole circuit to make sure it operates as intended.

# 2 Method

## 2.1 Design

### 2.1.1 Determining $\beta$

To determine  $\beta$  the circuit shown in figure 1.  $R_C$  was set to  $3.9K\Omega$ .  $R_B$  was then chosen to make  $V_{CE} \approx 7.5V$ . The base current was calculated by measuring the voltage across  $R_B$  and using Ohms law, the same was done for the collector current. To work out  $\beta$  the formula

$$\beta = \frac{I_C}{I_B}$$

was used. This gave a value of  $\beta = 337$ .

 


Figure 1: Circuit used to determine  $\beta$

### 2.1.2 Common Emitter Amplifier

The first stage of the circuit is a common emitter amplifier to amplify the signal from the microphone to be processed by later stages. The transistor  $\beta$  was found to be  $\beta = 337$ . First the current  $I_C$  was calculated using the equation with  $V_C = 7.5V$  and  $R_3 = 3.9K\Omega$

$$I_C = \frac{15 - V_C}{R_3}$$

This equation gives an  $I_C$  value of  $I_C = 1.92mA$ .  $R_4$  is then calculated with the equation

$$R_4 = \frac{1.5}{I_E}$$

with  $I_e \approx I_c$  this makes  $R_4 = 781\Omega$ . To calculate the biasing resistors it is set that the current through the biasing resistors is  $10 \times I_B$ . The equation

$$R_2 = \frac{V_{BE} + V_E}{10 \times I_B}$$

This gives an  $R_2 \approx 40K\Omega$   $R_1$  can then be calculated with the equation.

$$R_1 = \frac{V_{CC} - V_B}{10 \times I_B}$$

This gives  $R_1 \approx 27K\Omega$

### 2.1.3 Bandpass Filter

The band pass filter uses a resonant LC circuit to set the filter characteristics. The resonant frequency of an LC circuit is given as

$$f = \frac{1}{2\pi\sqrt{LC}}$$

The capacitor that forms the resonant circuit is  $C5 = 1\mu F$  to calculate the value for  $L$  the equation is rearranged to

$$L = \frac{1}{(2\pi f)^2 C}$$

This gives  $L = 11.3mH$ . To calculate the number of turns on the inductor the equation

$$N = \sqrt{\frac{Ll}{\mu \times a}}$$

$L$  = Inductance,  $l$  = length of magnetic circuit,  $\mu$  = permeability and  $a$  = cross sectional area.

is used. This gives  $N = 61$  Turns.

 


Figure 2: Common emitter amplifier circuit diagram

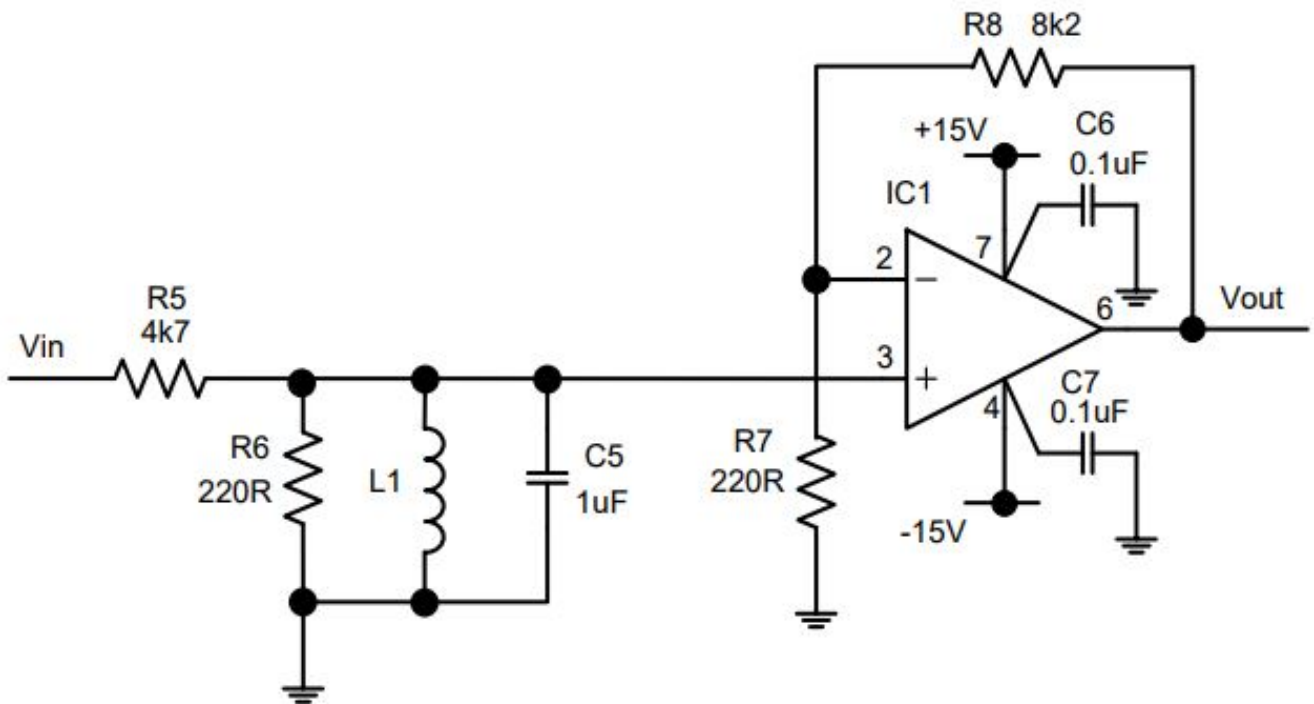


Figure 3: Band pass filter circuit diagram

#### 2.1.4 Code

The code was made to light all the LED's when maximum sound level was achieved. This was done with a logarithmic scale to allow high sensitivity at low sound levels but allow a large range of sound levels to be measured without clipping at high end values.

Number of bars lit	Voltage level(mV)
0	0
1	1.8
2	3.28
3	5.94
4	10.76
5	19.49
6	35.3
7	63.95
8	115.8
9	209
10	380

These values were then used to create the code shown in Listing 1

## 2.2 Construction

### 2.2.1 Common Emitter Amplifier

After the common emitter amplifier was constructed on bread board using the resistor values determined in the design stage. This was to determine that the amplifier had been designed correctly. To test the design the voltage between the transistor collector and ground was measured and was found to be  $V_C = 7.62V$ . This is within the allowable limit of 6V to 9V. The circuit was then constructed on the circuit board and the collector voltage was once again measured and found to be the same as before. The decoupling capacitors were then added to the circuit board. To test the amplifier a  $20mV_{Pk-Pk}$  sine wave at  $1kHz$  was applied to the input and the output measured on an oscilloscope. This is shown in figure 4. Using an input of  $23mV$  and an output of  $4.3V$  leads to a gain of  $G = 215$ .

 


Figure 4: Testing of the Common Emitter Amplifier

### 2.2.2 Band Pass Filter

To construct the band pass filter the Inductor must first be made. It was calculated that the required inductor would be made of 61 turns. This Inductor was created and its inductance was measured using an LCR meter. The desired inductance is  $11.3mH$  however the inductance was measured as  $11.9mH$ , to reduce this turns were removed and the Inductor re measured until its inductance was equal to  $11.3mH$ . This was achieved with 56 turns. The circuit was then constructed on the circuit board according to the circuit diagram shown in Figure 2.1.3. Once completed the filter was characterised between  $1Hz$  and  $5kHz$  with a  $2V_{Pk-Pk}$  sine wave input shown in figure 5.

## Band Pass Filter

 


Figure 5: Characterisation of Band Pass Filter

### 2.2.3 Signal Rectifier

The circuit shown in figure 6 was constructed on the circuit board and was then tested as shown in figure 7 with a  $1.5kHz$   $5V$  sine wave.

 


Figure 6: Rectifier Circuit Diagram

### 2.2.4 Low Pass Filter

The Low Pass Filter was constructed on the circuit board according to the circuit diagram shown in figure 8. After the circuit was constructed it was tested by inputting a  $1VPk - Pk$  sine wave as shown in figure 9. The filter was then characterised between  $1Hz$  and  $1kHz$  with a  $1VPk - Pk$  input sine wave shown in figure 10. The filter has a  $-3dB$  cutoff point at  $F_c \approx 80Hz$ .

### 2.2.5 PIC Microcontroller

The Microcontroller circuit was constructed according to the circuit diagram shown in figure 11. The PIC was then programmed with the code shown in the design phase shown in figure ??.

 


Figure 7: Rectifier analysis

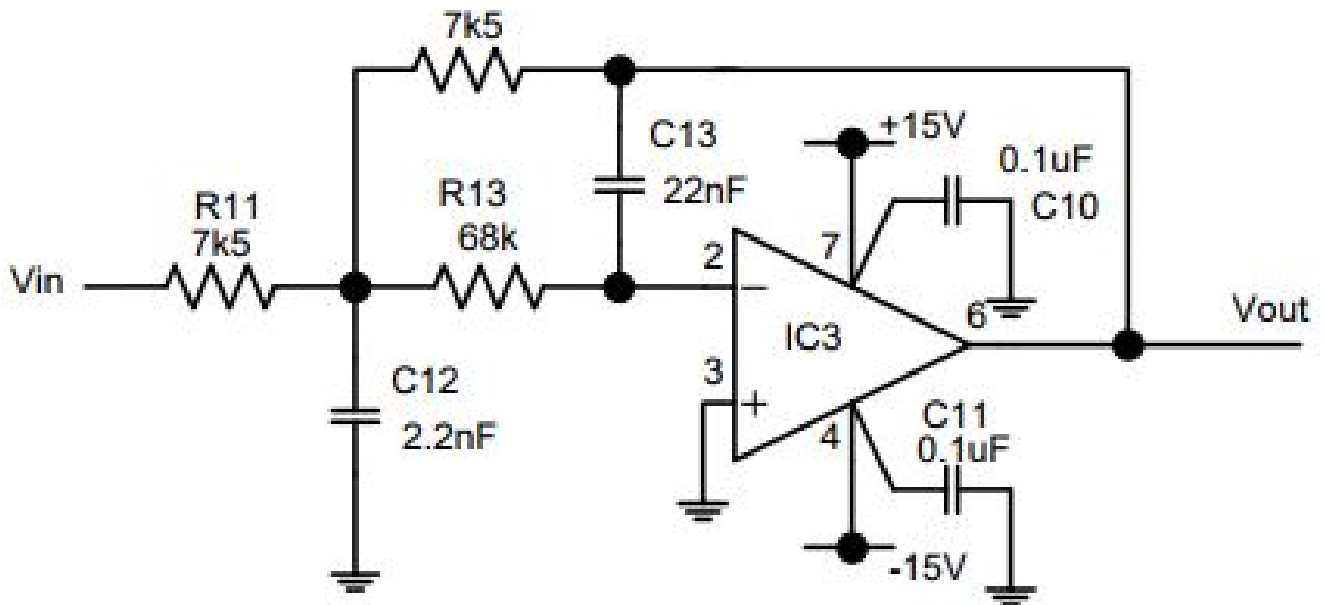


Figure 8: Low Pass Filter Circuit Diagram

### 2.2.6 Final Test

Once all parts of the circuit were connected together the meter was tested by playing a  $1.5kHz$  tone through a speaker from a signal generator near the meter and observing the LED's.

 


Figure 9: Low Pass Filter input &amp; output

 


Figure 10: Low Pass Filter Characterisation

### 3 Analysis



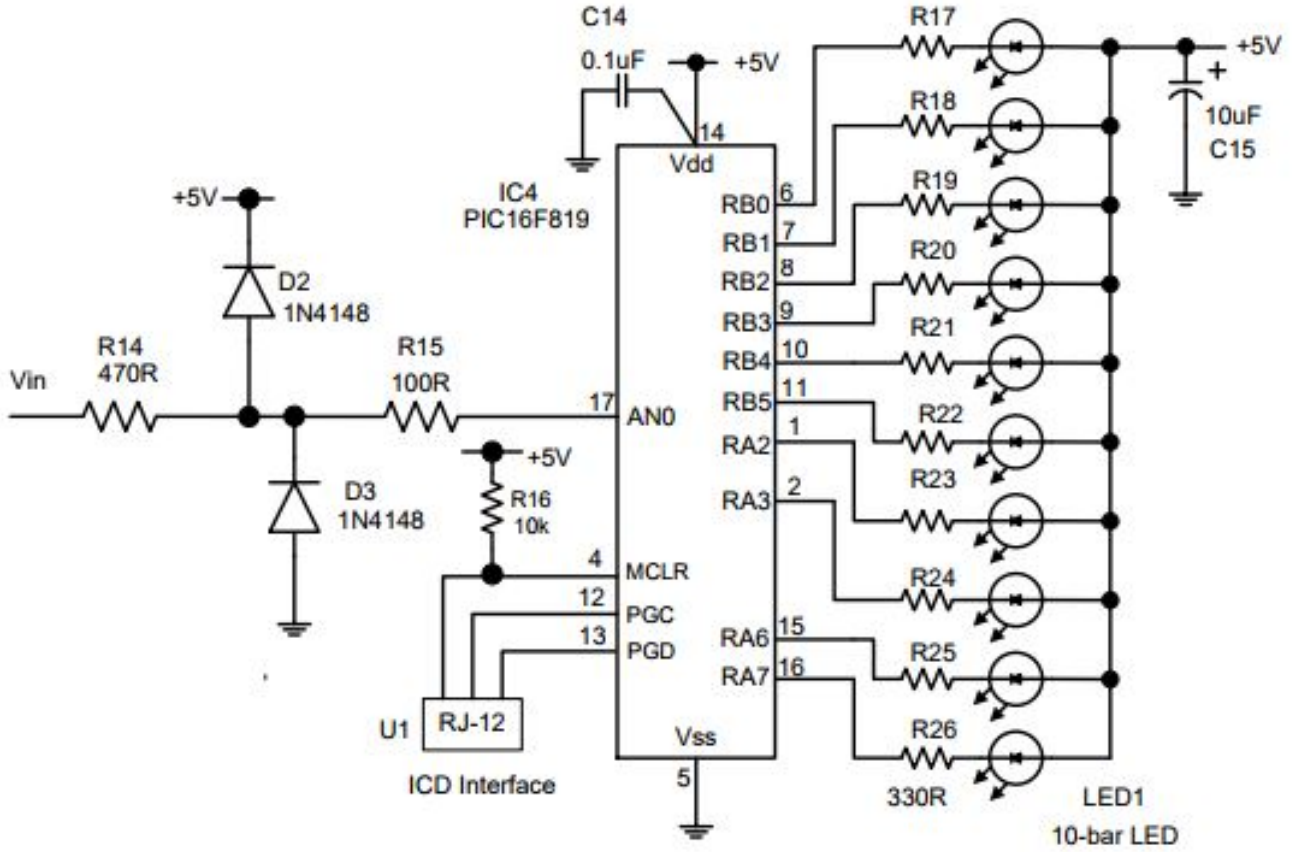


Figure 11: PIC Microcontroller circuit diagram

### 3.1 Finding $\beta$

The current gain of the transistor or  $\beta$  is the ratio of the collector current to the base current. This is because

$$I_c = \beta I_b$$

### 3.2 Common Emitter Amplifier

The Common Emitter Amplifier is used to amplify the low level signals coming from the microphone. This amplifier is used due to multiple attributes of the amplifier, namely, high input impedance, class A operation to prevent distortion and high single stage gain.

#### 3.2.1 Input Impedance

The high input impedance is needed as the microphone is a high impedance device and to allow maximum power transfer between the microphone and the amplifier  $Z_{mic} \approx Z_{amp}$ . If this were not the case the already small signal from the microphone would be reduced even more due to internal losses in the internal series impedance of the microphone. The input impedance of the amplifier can be calculated by looking at what impedance the input sees looking in to the input, this is  $R_1, R_2$  and the impedance looking in to the base all in parallel [2].  $R_1 = 270k\Omega, R_2 = 40k\Omega$  and the impedance looking in to the base is  $h_{fe} \times R_E$  as  $h_{fe}$  is equal to  $\beta$  [2]  $265k\Omega = 787(R_4)\Omega \times 337(\beta)$ . this works out to be

$$Z_{in} = \left( \frac{1}{270 \times 10^3} + \frac{1}{40 \times 10^3} + \frac{1}{265 \times 10^3} \right)^{-1} \approx 31k\Omega$$

The input capacitor  $C_1 = 10\mu F$  is in series with the input impedance of  $31k\Omega$ , the capacitor also forms a high pass filter with the input impedance

$$F_c = \frac{1}{2\pi RC} = 0.5Hz$$

[2] As the  $3dB$  cut-off point is  $0.5Hz$  almost all signal energy will be well above this point so the attenuation of this high pass filter can be ignored as it is negligible at frequencies of interest.

### 3.2.2 Output Impedance

The output impedance of the amplifier is calculated as the collector resistor in parallel with the resistance looking in to the collector. The resistance of the collector resistor is known as  $3.9k\Omega$  and the resistance looking in to the collector is the resistance of the transistor and the emitter resistor in series. As the transistor can be modelled as a current source there is a current source in series with  $R_E$ . A current source has impedance  $\approx \infty$ . The output impedance is therefore the  $3.9k\Omega$  resistor in parallel with a near infinite resistance so  $Z_{out} \approx 3.9k\Omega$ . This output impedance is low enough to allow good signal transfer to the next stage as the input impedance to the next stage is at least  $4.7k\Omega$  which is higher than the output impedance.

### 3.2.3 Biasing

The transistor is biased with  $R1$  and  $R2$ , These resistors are used to provide a constant quiescent current through the base and in turn from Collector to Emitter. This is done so that in the steady state the voltage at the collector with respect to ground is  $\approx 7.5V$ . This is done to allow the amplifier to produce positive and negative voltage swings. Without biasing the collector would be at  $15V$  in the steady state due to no quiescent current flowing through  $R1$  so no voltage drop across it. Due to this node being at  $15V$  the amplifier can only produce a negative voltage swing as this node is already at the highest voltage in the circuit so cannot go higher. If however this point is at  $7.5V$  half way between ground and  $V_{cc}$  then it can swing positive and negative in equal amounts. The capacitor  $C_2$  is used to remove the DC offset of the output so as to make the signal centred around  $0V$  instead of  $7.5V$ .

The resistors are chosen of values to allow the desired amount of quiescent current flows through the base. This is done by using a voltage divider configuration. This configuration however causes a design challenge that the current flowing through  $R2$  must be about ten times greater than the current flowing through the base to prevent this "load" on the voltage divider from lowering the voltage at its mid point and producing incorrect biasing.

### 3.2.4 Emitter Capacitor

The emitter capacitor  $C_3$  is chosen to allow stable biasing of the amplifier. Due to the relatively low emitter resistor of  $787\Omega$  the emitter voltage across  $R4$  can become small when compared to the voltage drop  $V_{BE}$  [2]. This leads to instability in the biasing and the quiescent voltage at the collector as  $V_{BE}$  varies with temperature. This change in  $V_{BE}$  with temperature causes changes in the base current with temperature. To solve this problem and still have an amplifier with high gain (Necessitating a low  $R_E$ ) a capacitor is placed in parallel with  $R_E$ . The capacitor is chosen so as to create the effect of a low impedance  $R_E$  at signal frequencies but the DC biasing signal only sees a high impedance  $R_4$  (as the capacitor has infinite impedance at DC), so as to prevent the instability aforementioned. The capacitor must be chosen so that at signal frequencies its impedance is low compared to  $r_e$  the resistance between base and emitter [2]. In this circuit the DC biasing signal sees  $\beta \times 787\Omega = 265k\Omega$  as the resistance looking in to the base, however at a frequency of  $1kHz$  an input signal looking in to the base would see  $787\Omega$  in parallel with  $\approx 0.5\Omega$  times  $h_{fe}$  or about  $168\Omega$ . This allows a low effective emitter resistor without the instability that this causes.

## 3.3 Band Pass Filter

The band pass filter section is formed from a parallel resonant circuit and a non inverting amplifier.

### 3.3.1 Parallel Resonant Circuit

The Parallel Resonant Circuit is formed from  $R6, L1 \& C5$ . The Parallel Resonant Circuit has a frequency response of  $0\Omega$  resistance at DC and infinite frequency as at DC the inductor is a short to ground and at infinite frequency the Capacitor is a short to ground. At the resonant frequency current flows backwards and forwards between the capacitor and inductor in phase with the input signal, this voltage opposes the input signal so no current can flow through the capacitor or inductor, as there is a voltage across the components but no current is flowing then the components must have infinite impedance from the perspective of the input signal. No current is drawn from the supply as  $I_L = -I_C$  so  $I_L + I_C = 0$  at resonance. For this particular circuit the resonant frequency is equal to

$$F = \frac{1}{2\pi\sqrt{LC}} = 1.5kHz$$

The circuit also has a property called  $Q$ . The  $Q$  factor is a representation of how damped the circuit is. Damping is a measure of the loss of energy from the circuit. A parallel LC circuit with ideal inductors and capacitors would have a  $Q = \infty$  as no energy is lost from the circuit and the resonant oscillations would continue forever. The higher the  $Q$  of the circuit the sharper the peak of resonance is meaning that a high  $Q$  circuit would transition from low impedance at frequencies not equal to the resonant to high impedance at the resonant frequency very quickly and then transition back to low impedance very quickly. The  $Q$  factor for this circuit is given by.

$$Q = \omega_0 RC = 2.07$$

 


Figure 12: Voltage against frequency for band pass filter

This means that the bandwidth of the filter is  $723Hz$  as bandwidth is equal to the resonant frequency divided by the  $Q$  factor. The  $3dB$  pass band for this filter is  $1140Hz$  to  $1860Hz$ . This however is not precise as the resonant circuit is also damped by the output impedance of the Common Emitter amplifier in series with  $R_5$  and the impedance of the Capacitor  $C_2$ . This however is much higher than the  $220\Omega$  resistor that is designed to damp the circuit so can be ignored as it is in parallel with the damping resistor. It can be seen from Figure 12 that the signal is phase shifted positively below the resonant frequency and negatively above the resonant frequency with  $0^\circ$  phase shift at the resonant frequency. This is because below the resonant frequency the circuit appears inductive and above the resonant frequency the circuit appears capacitive. The output of the filter is then fed in to a non inverting amplifier as this has a very high input impedance to prevent further loading of the resonant circuit. The amplifier has a gain given by

$$G = 1 + \frac{R_8}{R_7} \approx 38$$

### 3.4 Rectifier

The rectifier section is formed by a Diode to allow current to flow only in one direction and a unity gain buffer to provide a low impedance drive to the next stage

#### 3.4.1 Diode

The Diode only allows current to flow in one direction. This diode only allows negative voltages to be passed, this can be seen in figure 7 as the output only has negative peaks but the input has both negative and positive peaks but the diode removed them due to it blocking forward current flow.

#### 3.4.2 Unity Gain Buffer

The unity gain buffer is used to provide a low impedance output for this stage of the circuit. The unity gain buffer works by using negative feedback to reduce the gain of the op-amp to 1. The op-amp has very high input impedance  $Z \approx 10^7\Omega$  to prevent loading prior stages and to provide a low impedance source to further stages. The feedback is provided through feedback resistor  $R_{10}$ .  $R_9$  is used as a pull down resistor to prevent a positive voltage when the diode is reverse biased. Due to the high input impedance the low reverse bias current  $I \approx 10^{-9}A$  would create a voltage across the high input impedance as  $V = IR$ , even though  $I$  is small  $R$  is large so a voltage is still created so causing the op amp output to rise.  $R_9$  is used to lower the input impedance by putting it in parallel with the input impedance.

### 3.5 Low Pass Filter

The low pass filter is used to smooth the rectified waveform to a near constant DC level that is approximately equal to the peak value of the rectified waveform. The filter works by using negative feedback proportional to the frequency. This is done by using a capacitor as a feedback element. The filter also uses  $C_{12}$  and  $R_{11}$  to form an RC low pass filter.

### 3.5.1 Variable Feedback

The filter uses an inverting op-amp amplifier with negative feedback determined by the  $7.5K\Omega$  resistor and the capacitor  $C13$ . At DC the capacitors impedance is  $\infty$  so the feedback is just  $7.5K\Omega$ .

$$G = -\frac{R_f}{R_{in}}$$

[1] at DC this means the gain is equal to  $-1$  as the feedback impedance and the input resistor are the same. At higher frequencies the impedance of the capacitor becomes lower so the feedback impedance becomes lower as the feedback resistor and capacitor are in parallel. This lowering of the feedback impedance as the input resistor stays constant reduces the gain as the modulus of the gain is proportional to the feedback resistor.

### 3.5.2 RC Filter

The resistor  $R11$  and  $C12$  form an RC low pass filter. The filter works on the principle of a frequency dependent voltage divider.

$$V_{out} = \frac{Z_c}{Z_c + R_{11}} \times V_{in}$$
$$F_0 = \frac{1}{2\pi RC}$$

At low frequencies the capacitor has high impedance so the fraction is approximately equal to 1. At high frequencies the capacitor has low impedance so the value for the fraction is low so the signal is attenuated. Both of these low pass filter circuits combine their attenuation of high frequencies so creating a steeper roll-off. this roll-off can be seen in Figure 10. Low frequencies have a gain of close to or greater than 1 whereas high frequencies have a gain much lower than 1.

## 3.6 PIC Microcontroller

The PIC microcontroller uses two diodes  $D2$  and  $D3$  as input protection diodes. If the input is less than  $\approx -0.6V$  then current flow through  $D3$  clamping the voltage at  $-0.6V$ . If the input goes higher than  $5.6V$  then current flows through  $D2$  and the voltage is clamped at a maximum of  $5.6V$ . This is to protect the input of the PIC from over voltage.

### 3.6.1 Code

The code uses the ADC of the PIC to produce a value between 0 and 1023 for an input of 0 to  $5V$ . This value is then used with a series of IF statements to determine how many LED's should be on depending on the input value. The number of LED's on at any time is determined by a Log function. This allows greater resolution at low sound levels such as quiet talking but allow a high range of sounds to be measured such as loud blowing on the microphone without the LED graph peaking too early. The LED output uses two registers as one register can only support 6 LED's but there are 10 LED's on the LED bar graph.

## 4 Conclusion

In conclusion the system works as intended. The system was sensitive to low sounds but did not overload with loud sounds. The system works by using a high gain amplifier to amplify the signals coming from the microphone and then a band pass filter to filter the frequencies of interest and a rectifier and low pass filter to create a DC level proportional to the sound level. This is then fed in to a PIC micro controller to control the LED's depending on the sound level signal. All objectives have been met in this Lab however if I were to do this lab again I would remember to put  $R0$  in as I spent a long time debugging the circuit thinking it did not work however I had forgotten  $R0$ . In future I will remember to check the circuit diagram and make sure that I have included all components before assuming that the circuit has a fault. I would also make sure to center Oscilloscope traces and to turn measurements on.

## 5 Appendix

Listing 1: PIC Code

```
1 //Newcastle University – EEE – Stage 1 – Sound Level Meter
2 //16F819 PIC software to drive a 10-LED bargraph display from a dc level on ADC input 0 (AN0).
3 //Port A and B used to drive LEDs.
4 //Pin Configuration:
5 //Pin Configuration:
```

```

6 //1-RA2 (LED4) 18-NC
7 //2-RA3 (LED3) 17-AN0 (DC Sound Level input)
8 //3-NC 16-RA7 (LED1)
9 //4-MCLR 15-RA6 (LED2)
10 //5-VSS 14-VDD
11 //6-RB0 (LED10) 13-RB7 (PGD)
12 //7-RB1 (LED9) 12-RB6 (PGC)
13 //8-RB2 (LED8) 11-RB5 (LED5)
14 //9-RB3 (LED7) 10-RB4 (LED6)
15 #include <xc.h> //header file for device
16 #include <stdint.h> //header file for standard types e.g uint8_t
17 //fuse settings to configure device
18 //i.e. NOWDT - No Watchdog Timer, INTOSCIO - Internal clock used, pins available for I/O
19 #pragma config MCLRE = ON, CP = OFF, CPD = OFF, BOREN = OFF, WDIE = OFF
20 #pragma config PWRITE = OFF, FOSC = INTOSCIO, LVP = OFF, DEBUG = ON
21 void main()
22 {
23     /*** INSERT ANY VARIABLE DECLARATIONS HERE ***/
24     uint8_t = 8-bit unsigned number
25     uint16_t = 16-bit unsigned number
26     uint16_t value;
27     /*** The following code initializes the PIC ***/
28     OSCCONbits.IRCF = 0b111; //use internal 8MHz clock (FOSC=8MHz)
29     TRISB = 0b00000000; //Port B all outputs
30     TRISA = 0b00110011; //Port A B6/B7/B3/B2 outputs
31     ADCON1bits.ADFM = 1; //A/D Result Format Right Justified
32     ADCON1bits.ADCS2 = 1; //A/D clock Source divided by 2
33     ADCON1bits.PCFG = 0b1110; //Enable AN0 input for sound level ADC
34 13
35     ADCON0bits.ADCS = 0b01; //set ADC clock, should be between 1.6us and 6.4us (1/8MHz x 16 = 2us)
36     ADCON0bits.CHS = 0b000; //select AN0 for input
37     ADCON0bits.ADON = 1; //A/D Converter is operating
38     do
39     {
40         //The code below will read the digital value from the 10-bit analogue to digital converter.
41         //The range of the return value will be between 0 and 1023. Where 0V = 0 and 5V = 1023.
42         //For example 2.5V on the ADC will return 511 to the variable value below.
43         ADCON0bits.GO_DONE = 1; //start A/D conversion
44         while(ADCON0bits.GO_DONE == 1); //wait for A/D conversion to complete
45         value = ADRESH; //read MSB of ADC result
46         value = value << 8; //shift left 8 bits
47         value = value + ADRESL; //read LSB of ADC result. value now contains a 10-bit ADC number
48         /*** INSERT YOUR PROGRAM CODE HERE TO ILLUMINATE THE LEDS***/
49         //The basic requirement of your code is:-
50         //(i) To use the variable value to determine which LED bars should be switched on.
51         //(ii) To write the appropriate code to the output pins RB0-RB5 and RA2,RA3,RA6,RA7.
52         //The PIC PORTA and PORTB registers should be used to output a value to the Port pins
53         //PORTA=0b00001111; will output a binary number to port A. Bits 7,6,5,4=0 and Bits 3,2,1,0=1.
54         //Alternatively PORTA=15; for decimal equivalent.
55         //The parameter may also be a variable instead of a constant e.g. PORTA=value;
56
57         if(value == 0){
58             PORTA=0b11111111
59             PORTB=0b11111111
60         }
61     }
62
63     if(value > 0 && value <= 1.8){
64         PORTA=0b01111111
65         PORTB=0b11111111
66     }
67
68
69     if(value > 1.8 && value <= 3.28){
70         PORTA=0b00111111
71         PORTB=0b11111111
72     }
73
74
75     if(value > 3.28 && value <= 5.94){
76         PORTA=0b00110111
77         PORTB=0b11111111
78     }
79
80
81     if(value > 5.94 && value <= 10.76){
82         PORTA=0b00110011
83         PORTB=0b11111111
84     }
85 }
86

```

```

87 if(value > 10.76 && value <= 19.49){
88 PORTA=0b00110011
89 PORTB=0b11011111
90
91 }
92
93 if(value > 19.49 && value <= 35.3){
94 PORTA=0b00110011
95 PORTB=0b11001111
96
97 }
98
99 if(value > 35.3 && value <= 63.95){
100 PORTA=0b00110011
101 PORTB=0b11000111
102
103 }
104
105 if(value > 63.95 && value <= 115.8){
106 PORTA=0b00110011
107 PORTB=0b11000011
108
109 }
110
111 if(value > 115.8 && value <= 209){
112 PORTA=0b00110011
113 PORTB=0b11000001
114
115 }
116
117 if(value > 115.8 && value <= 380 ){
118 PORTA=0b00110011
119 PORTB=0b11000000
120
121 }
122
123
124
125
126
127
128
129
130
131
132 } while (1);
133 }

```

## References

- [1] Bernard Grob. *Basic electronics*. eng. 1st metric ed.. New York: McGraw-Hill, 1987. ISBN: 0071004432.
- [2] Paul Horowitz. *The art of electronics*. eng. 2nd ed.. Cambridge [England] ; New York: Cambridge University Press, 1989. ISBN: 0521370957.